

WORKSHOP CALCULATION AND SCIENCE-UNIT 7: BASIC ELECTRICITY

SEMESTER : I

1. Which machine converts mechanical energy into electrical energy?

- a) Battery b) generator c) heater d) iron box

Ans: generator

2. What is the unit of current?

- a) Ampere b) volt c) ohm d) watt

Ans: ampere

3. What is the unit of resistance?

- a) Ampere b) volt c) ohm d) watt

Ans: ohm

4. What is the flow of electrons in any conductor?

- a) Voltage b) current c) resistance d) power

Ans: current

5. Which property of a substance is opposing the flow of electric current?

- a) Current b) voltage c) resistance d) EMF

Ans: resistance

6. Which is very good conductor?

- a) Copper b) cast iron c) wrought iron d) steel

Ans: copper

7. Which is mineral insulator?

- a) Glass b) quartz c) mica d) porcelain

Ans: mica

8. What is the total resistance if three resistances 3 ohms, 9 ohms and 5 ohms are connected in series?

- a) 11 ohms b) 7 ohms c) 17 ohms d) 1/17 ohms

Ans: $R_1 = 3 \text{ Ohms}; R_2 = 9 \text{ Ohms}; R_3 = 5 \text{ Ohms};$

$R = R_1 + R_2 + R_3 = 3 + 9 + 5 = \mathbf{17 \text{ Ohms}}$ (Series connection)

9. What is the total resistance if two resistances of 4 ohms and 6 ohms are connected in parallel?

- a) 2.4/10 b) 24/10 c) 10/24 d) 10/2.4

Ans: $R_1 = 4 \text{ Ohms}; R_2 = 6 \text{ Ohms};$

(Parallel connection) $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{4} + \frac{1}{6} = \frac{10}{24};$

$R = \frac{24}{10} = \mathbf{2.4 \text{ Ohms}}$

WORKSHOP CALCULATION AND SCIENCE-UNIT 7: BASIC ELECTRICITY

10. What is the total resistance if three resistances of 4 ohms, 6 ohms and 8 ohms respectively are connected in parallel?

- a) 24 b) 13 c) 24/13 d) 13/24

Ans: $R_1 = 4 \text{ OHMS}$, $R_2 = 6 \text{ OHMS}$, $R_3 = 8 \text{ OHMS}$;

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{4} + \frac{1}{6} + \frac{1}{8} = \frac{6+4+3}{24} = \frac{13}{24}$$

R = 24/13 Ohms

11. Which is same in series connection of resistors in circuit?

- a) Current b) voltage c) resistance d) power

Ans: current

12. Which law states that at constant temperature the current passing through a closed circuit is directly proportional to the potential difference and inversely proportional to the resistance?

- a) Ohms law b) lenz law c) newtons law d) hookes law

Ans: ohms law

13. What is the resistance? $I = 11.5 \text{ Amps}$, $V = 380 \text{ Volts}$, $R = \dots\dots\dots \text{ Ohms}$?

- a) 13 ohms b) 23 ohms c) 33 ohms d) 43 ohms

Ans: $R = \frac{V}{I} = \frac{380}{11.5} = \mathbf{33 \text{ ohms}}$

14. What is the current? $R = 50 \text{ Ohms}$, $V = 220 \text{ Volts}$, $I = \dots\dots\dots \text{ Amps}$

- a) 4.1 amps b) 4.2 amps c) 4.3 amps d) 4.4 amps

Ans: $I = \frac{V}{R} = \frac{220}{50} = \mathbf{4.4 \text{ ohms}}$

15. What is the voltage? $R = 250 \text{ Ohms}$, $I = 0.44 \text{ Amps}$, $V = \dots\dots\dots \text{ Volts}$

- a) 100 ohms b) 105 volts c) 108 volts d) 110 volts

Ans: $V = I \times R = 0.44 \times 250 = \mathbf{110 \text{ volts}}$

16. Which statement is correct according to ohm's law?

- a) $I = \frac{1}{V}$ b) $I = R$ c) $I = \frac{V}{R}$ d) $I = \frac{R}{V}$

Ans: $I = \frac{V}{R}$

17. What is the filament resistance if a 6 volt bulb draws a current of 0.5 amps?

- a) 12 Ω b) 10 Ω c) 3 Ω d) 1.2 Ω

Ans: $R = \frac{V}{I} = \frac{6}{0.5} = \mathbf{12 \Omega}$

18. How much watt second in 1 watt hour?

- a) 1000 watt sec b) 2000 watt sec c) 3600 watt sec d) 4000 watt sec

Ans: 3600 watt sec

WORKSHOP CALCULATION AND SCIENCE-UNIT 7: BASIC ELECTRICITY

19. What is the power if an emf of one volt causes a current flow of 1 ampere?

- a) 1 watt b) 1 kilowatt c) 1 HP d) 1 kilowatt hour

Ans: 1 watt

20. Which is equal to electric power?

- a) R^2I watts b) I^2R Watts c) $\frac{R^2}{I}$ watts d) $\frac{I^2}{R}$ watts

Ans: I^2R Watts

21. How much power does it consume if an electric heater draws a current of 10 amps at 200 volts?

- a) 2000 watts b) 2010 watts c) 2020 watts d) 2030 watts

Ans: $I = 10$ amps; $V = 200$ Volts;
 $P = V \times I = 200 \times 10 = \mathbf{2000 \text{ Watts}}$

22. What is the resistance of an electric iron if the rating of electric iron is 220V and 500 watts?

- a) 94.8 ohms b) 95.8 ohms c) 96.8 ohms d) 97.8 ohms

Ans: $V = 220V$; $P = 500$ Watts;
 $R = V^2/P = 220^2/500 = \mathbf{96.8 \text{ OHMS}}$

23. What is the voltage of the immersion heater? $P = 500$ Watts; $I = 2.27$ amps; $V = \dots\dots\dots$ volts?

- a) 200.3 volts b) 210.3 volts c) 220.3 volts d) 230.3 volts

Ans: $V = \frac{P}{I} = \frac{500}{2.27} = 220.26 = \mathbf{220.3 \text{ volts}}$

24. What is the unit of intensity of magnetic field?

- a) Wb/m b) m/wb c) Hertz d) Coloumb

Ans: wb/m

25. Which law states about electromagnetic induction?

- a) Ohm's law b) hooke's law c) lenz's law d) Faraday's law

Ans: Faraday's law

26. What is the formula for induced emf?

- a) $B^2L \sin\theta$ volts b) $BL \sin\theta$ volts c) $BLV \sin\theta$ volts d) $B^2V \sin\theta$ volts

Ans: $BLV \sin\theta$ volts

27. What does EMF stands for?

- a) Electronic magnetic force b) Electro motive force
c) Electromagnetic force d) Electromated force

Ans: electro motive force

28. Which is the example for statically induced emf?

- a) Generator b) motor c) transformer d) refrigerator

Ans: transformer

WORKSHOP CALCULATION AND SCIENCE-UNIT 7: BASIC ELECTRICITY

29. Which is the example of dynamically induced Emf?

- a) Motor b) generator c) car d) motor bike

Ans: generator

30. Which is the unit electrical power?

- a) Volts b) ohms c) watts d) ampere

Ans: watts

31. What is the current flow in the bulb? $P=550$ Watts; $R = 22$ Ohms; $I = \dots\dots\dots$ amps?

- a) 2 amps b) 3 amps c) 4 amps d) 5 amps

Ans: $I^2 = \frac{P}{R}$;
 $I = \sqrt{550/22} = 5 \text{ Amps}$

32. What is the power required? $I = 0.455$ Amps, $R = 484$ Ohms, $P = \dots\dots\dots$ Watts?

- a) 98.2 watts b) 99.2 watts c) 100.2 watts d) 101.2 watts

Ans: $P = I^2R = (0.455)^2 \times 484 = 100.2 \text{ Watts}$

33. What is the rated power if an adjustable resistor bears the following label 1.5 ohms/ 0.08A?

- a) 9.2 watts b) 9.4 watts c) 9.6 watts d) 9.8 watts

Ans: $P = I^2R = (0.08)^2 \times 1500 = 9.6 \text{ Watts}$

34. How much voltage will be required to illuminate a 40 watts fluorescent lamp draws a current of 0.10 amperes?

- a) 390 volts b) 395 volts c) 400 volts d) 405 volts

Ans: $V = \frac{P}{I} = \frac{40}{0.10} = 400 \text{ volts}$

35. How many hours will take for a 100 watts bulb to consume 1 kwh energy? $W = 1$ KWH, $P = 100$ Watts, $t = \dots\dots\dots$ hours?

- a) 10 hours b) 12 hours c) 18 hours d) 24 hours

Ans: Given Work = 1KWH = 1000 WH; Power = 100 Watts;

Work = Power x Time;

Time = $\frac{WORK}{POWER} = \frac{1000}{100} = 10 \text{ hours}$